


Total number of printed pages-8

3 (Sem-3/CBCS) PHY HC 3

2022

PHYSICS

(Honours)

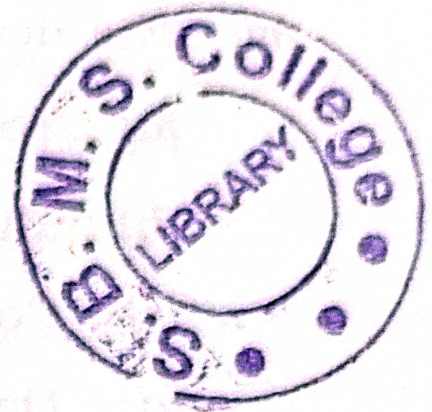

Paper : PHY-HC-3036

**( Digital Systems and Applications )**

Full Marks : 60

Time : Three hours

**The figures in the margin indicate full marks for the questions.**

1. Answer the following questions as directed :

**(any seven)**

1×7=7

(i) The deflection sensitivity of a CRO can be enhanced by reducing \_\_\_\_\_.

(Fill in the blank)

Contd.

(ii) The intel 8085 microprocessor is a 16 bits processor.

(State True or False)

(iii) The design of flip-flops are based on


- (a) Sequential logic
- (b) Multiplexing
- (c) Combinational logic
- (d) Demultiplexing

(Choose the correct option)

(iv) The full form of MDR is \_\_\_\_\_.

(Fill in the blank)

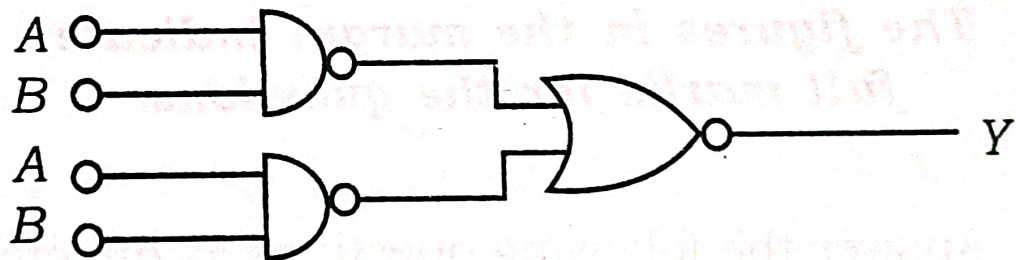(v) For the given circuit diagram, the output Y is



(a)  $A + B$

(b)  $AB$

(c)  $\overline{A + B}$

(d)  $\overline{A.B}$

(Choose the correct option)

(vi) The storage capacity of each stage in a shift register is \_\_\_\_\_ bits.

*(Fill in the blank)*

(vii) Monostable multivibrators can be used as frequency divider by using

(a) Sawtooth wave generator

(b) Triangular wave generator

(c) Sine wave generator

(d) Square wave generator

*(Choose the correct option)*

(viii) What is the full form of VLSI?

(ix) Mention *one* advantage of a digital circuit over an analog circuit.

(x) Write the names of an active component and a passive component in a circuit.

(xi) Convert the binary number  $101.11_2$  into decimal number.

(xii) Convert the decimal number 54.50 into binary number.

2. Answer the following questions in brief :  
(any four)  $2 \times 4 = 8$

(i) Convert the following hexadecimal numbers to binary

(a) B32

(b) AE2.4

(ii) Reduce the following Boolean function

$$\overline{A}\overline{B} + \overline{A}B + AB + \overline{A}\overline{B}$$

(iii) Using 2's complement, perform the subtraction

$$101.1101 - 101.0111$$

(iv) What do you mean by D/A converter? Name *two* types of D/A converter.

(v) What is synchronous counter? Write *two* basic applications of counters.

(vi) What is Primary memory? What is its function?

(vii) Draw the logic symbol of XOR gate and construct the truth table.

(viii) Mention *two* applications of Multiplexers.

3. Answer **any three** questions from the following :

5×3=15

(i) (a) Convert the following Boolean expression into standard SOP form

$$A + \bar{B} + CA$$

(b) Show that  $(\overline{AC} + B)(\overline{A + C}) = BAC$

(ii) Explain how SR flip-flop is obtained from using NAND gates. Draw the truth table.

(iii) With neat diagram explain the working of a serial-in parallel-out shift register. What is the basic difference between a shift register and a counter?

(iv) Simplify the Boolean function  $F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$  with the help of K-maps.

(v) Write short notes on : (**any one**)

(a) BCD decade counter

(b) Astable Multivibrator

(c) Clocked D flip-flop

(vi) Define Opcode and Operand. Write an 8085 Assembly Language Program (ALP) to store data of register C into memory location 2054H. 2+3=5

(vii) Prove the following equations with the help of truth tables :

$$(a) \quad \overline{A+B} = \overline{A} \cdot \overline{B}$$

$$(b) \quad \overline{A \cdot B} = \overline{A} + \overline{B}$$

(viii) Using NAND gates only, realize the following gates :

(a) AND

(b) OR

(c) NOT

4. Answer **any three** of the following questions:  $10 \times 3 = 30$

(i) What are decoders and encoders ? With the help of a logic diagram and truth table explain.  $2+4+4=10$

(a) 2 to 4 decoder

(b) Octal to binary encoder.

(ii) What is a full Adder ? Draw the block diagram and truth table of a full Adder. Design a full Adder logic circuit by applying Karnaugh map.  $1+4+5=10$

(iii) (a) Draw the K-map to minimize the following expression.

$$\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + \overline{A} B C + A \overline{B} \overline{C}$$

- (b) For the given truth table, find the minimized logical expression by the use of K-map and SOP method and draw the equivalent logic circuit:  
4+6=10

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- (iv) With the help of a logic diagram and function table explain  
5×2=10

(a) 1 to 2 Demultiplexer

(b) 2 to 1 Multiplexer.

- (v) Draw the block diagram of a CRO. What is the function of electron gun in a CRO? Explain how the phase difference between two sinusoidal voltages of the same frequency and same amplitude can be determined by using CRO.

3+2+5=10

(vi) What is a microprocessor? What is the difference between microprocessor and microcomputer? Write the basic features of Intel 8085 microprocessor.

1+1+8=10

(vii) (a) Give the symbol and truth table of XNOR gate.

(b) Realize the NOT gate using transistor.

(c) What are preset and clear operations? 3+3+4=10

(viii) (a) What do you mean by the following terms used in a Microprocessor?

(i) Buses

(ii) Registers

(iii) ALU

(b) What is a Half Subtractor? Give the symbol and the truth table.

6+4=10